



Lecture 2: Switches, Rectifiers and Generators

Topics:


- 1) Homework Review
- 2) Switches
- 3) Bridge Rectifiers
- 4) AC vs. DC
- 5) Function Generators and Oscilloscopes

Homework Review:

Homework 1: Voltage dividers

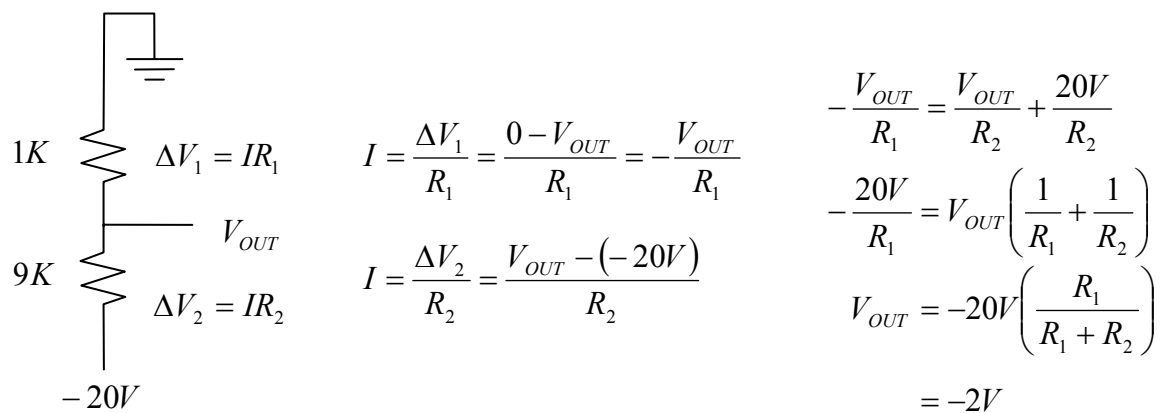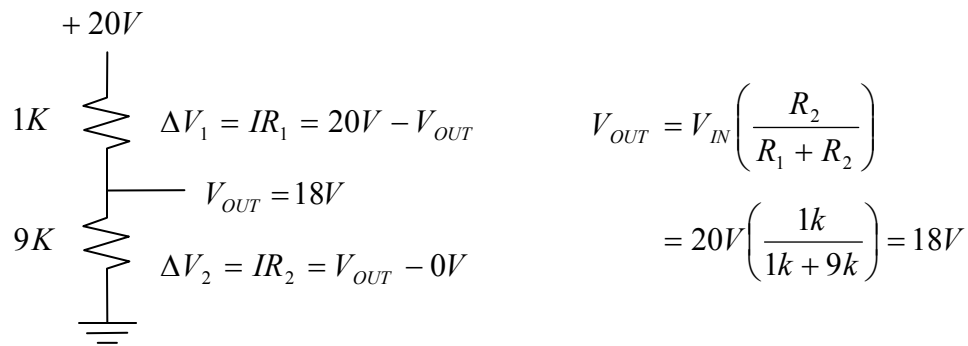

Homework 2: Diodes

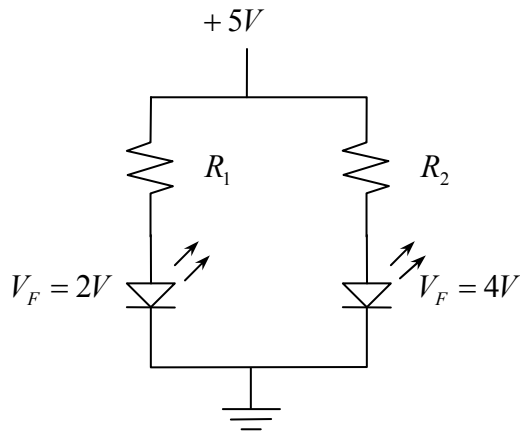


$$R_1 = \frac{(5V - 2V)}{20mA} = 150\Omega$$

$$R_2 = \frac{(5V - 4V)}{20mA} = 50\Omega$$


There are two diodes that will be used in class:

- Zener diodes: If you put a negative voltage across a Zener diode, it has a second turn-on point. The slope of the I-V curve of the second turn-on point is even more abrupt than the slope of the I-V curve of the first turn-on point. You can tailor the breakdown voltage from a couple of volts to hundreds of volts. A Zener diode is used in reverse bias to clamp and hold the voltage. The name Zener diode comes from a Physics term called the Zener effect, which is not even related to the Zener diode at all. However, the Zener diode does exhibit the Avalanche effect.
- Silicon diodes: These diodes do not emit light. Have same functionality as other diodes. Their forward voltages are really small ($\sim 0.6-0.7$ volts).

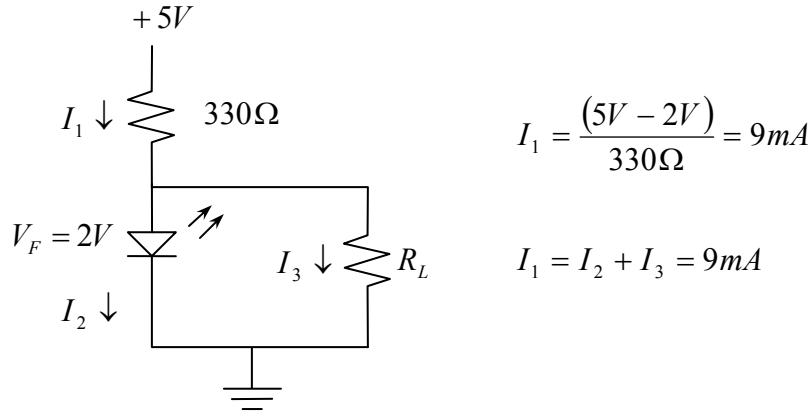Diodes don't have resistance. If the voltage is below a diode's forward voltage, then the element looks like an open circuit. If the voltage is above the forward voltage, the element behaves as a short circuit.



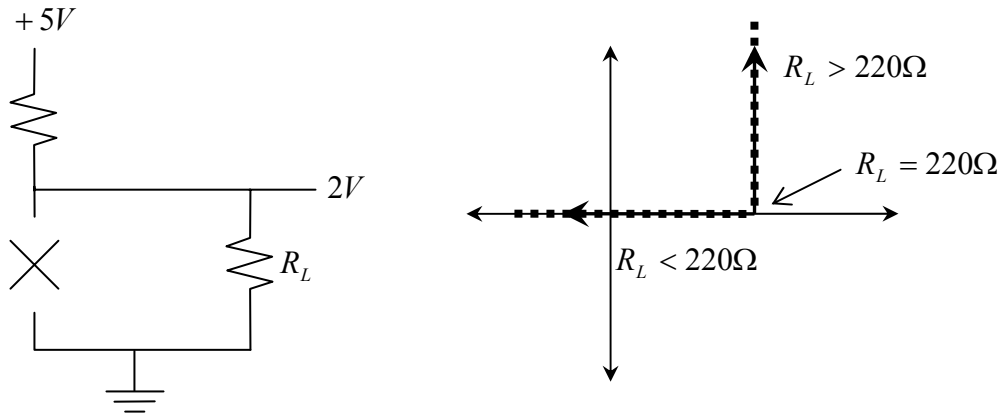If R_L is such that $V_{OUT} = 1V$, there is no current flow through the diode. The diode conducts (turns on) when V_{OUT} hits R_L .




One gets $V_{OUT} = 2V$ when $R_L = 220$ ohms.

Now, try $R_L = 330$ ohms. The voltage divider predicts $V_{OUT} = 2.5V$. BUT the diode clamps at 2.0V! The diode will steal any necessary current to stay at 2V. The bigger R_L is, the more current passes through the diode.

AC vs. DC

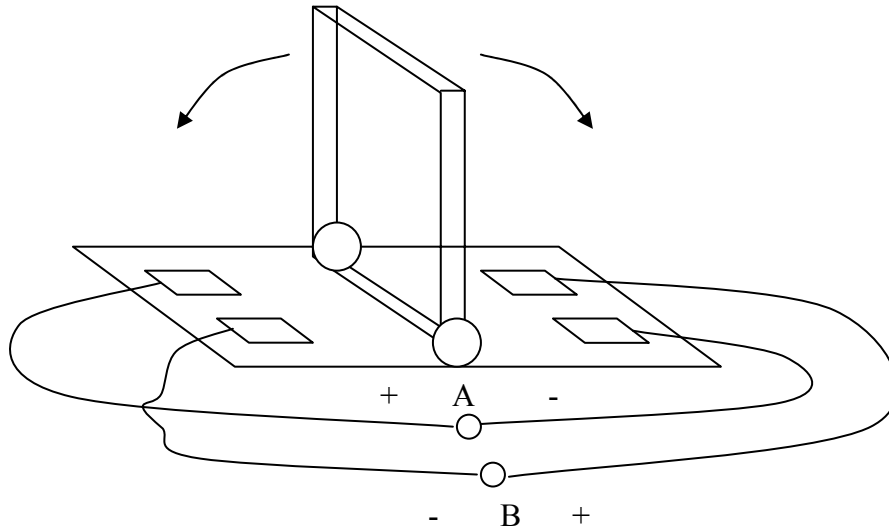One can implement a simple DC to AC converter with a switch configuration like the following:




With switch to one position:

$$V_A - V_B = 9V$$

With switch on the other position:

$$V_B - V_A = -9V$$

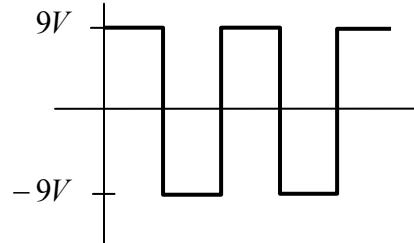

MIT OpenCourseWare
<http://ocw.mit.edu>

EC.S06 / EC.S11 Practical Electronics
Fall 2004

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.