

### 6.013 – Electromagnetics and Applications


**Problem Set 6 (five problems)**

---

**Suggested Reading:** Course notes, Sections 7.1.1-7.1.2, 7.2.1-7.2.2, 8.1, 8.3.1

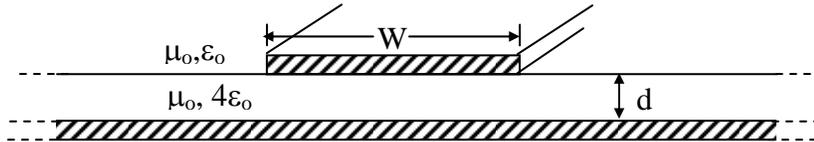**Problem 6.1**

Stripline can be approximated as an ideal parallel-plate TEM line if its width  $W$  is much greater than the separation  $d$  between top and bottom plates (i.e., if fringing fields can be neglected). Consider the illustrated infinitely long stripline for which  $d = 1$  micron and the medium between the plates has  $\mu = \mu_0$  and  $\epsilon = 4\epsilon_0$ .




- For what width  $W$  is the impedance of this line  $50\Omega$ ? Is the ideal parallel plate model valid for these dimensions? Discuss briefly.
- For a 1-volt DC signal, what is the intensity  $I$  (time-average Poynting vector magnitude [W]) of the TEM electromagnetic field propagating between the plates?
- Evaluate the time average electric and magnetic energy densities per meter, i.e.,  $W_e$  and  $W_m$  [J/m], on this line for case (b) (neglect fringing fields).
- Show that the average power on the line,  $c_{\text{line}}(W_e + W_m)$ , equals the  $I$  found in (b).
- Show that if two arbitrary signals flowing in opposite directions are superimposed so that  $v(z,t) = f_+(t - z/v) + f_-(t + z/v)$ , then the total power flowing down this line in the  $+z$  direction at any  $(t,z)$  equals the power flowing in the  $+z$  direction minus the power flowing in the  $-z$  direction. Show whether or not such superposition of powers also applies when the two signals flow in the same direction on TEM lines.

**Problem 6.2**


A 30-centimeter-long, air-filled  $100\Omega$  TEM line is excited at one end by a matched voltage source  $V(t)$ , where  $V(t)$  is a step function  $2u(t)$  volts. Sketch and quantitatively dimension  $V(z)$  and  $I(z)$  on the line at  $t = 15 \times 10^{-10}$  sec for the case where the load is:

- a  $300\Omega$  resistor
- a capacitor  $C = 2 \times 10^{-12}$  F
- a diode back-biased with a 1-volt battery, as shown.

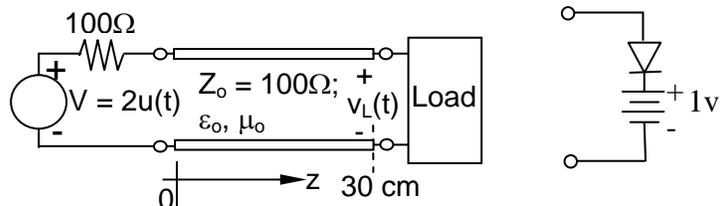

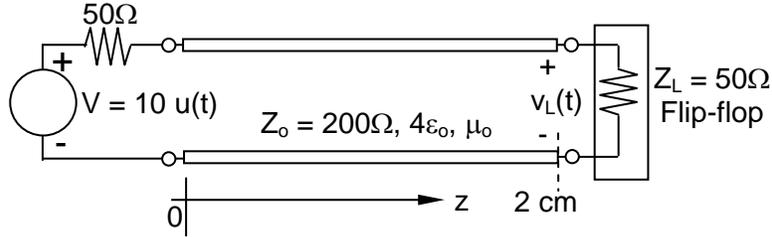**Problem 6.3**

A line driver at one end of a 2-cm long 200-ohm TEM transmission line triggers a flip-flop at the other end with a step function, as illustrated. The dielectric in the line has  $\epsilon = 4\epsilon_0$  and  $\mu = \mu_0$ .




- (a) Sketch and dimension  $v(t,z)$  on the line at  $t = 0.1 \text{ ns}$  ( $10^{-10}$  sec).
- (b) Repeat (a) for  $t = 0.2 \text{ ns}$ .
- (c) Sketch quantitatively the load voltage  $v_L(t)$  until the flip-flop is triggered; its trigger voltage is 4 volts. Note that triggering is excessively delayed.
- (d) What is the asymptotic value of the load voltage  $v_L(t)$  as  $t \rightarrow \infty$ ?
- (e) If the line impedance were matched at 50 ohms, would there still be excessive delay?
- (f) Write a simple equation for  $v(z,t)$  valid for  $0 < t < 0.1 \text{ ns}$ , then extend it to 0.2 ns.

**Problem 6.4**


A unit-step current source  $I_0(t) = u(t)$  directly drives the illustrated circuit. Sketch and dimension the voltage  $v(z)$  on all lines at:

- (a)  $t = D/2c$
- (b)  $t = 3D/2c$
- (c)  $t = 5D/2c$ .

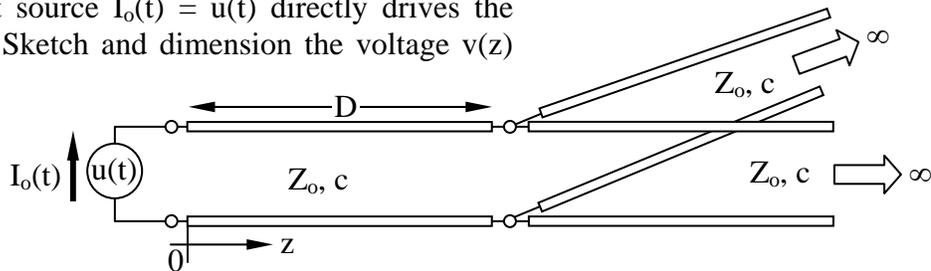

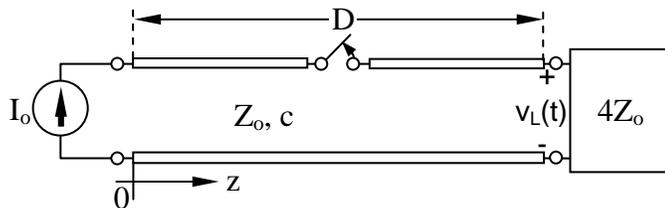**Problem 6.5**

A current source  $I_0$  drives a delicate transistor that has an input impedance of  $4Z_0$  through a TEM line of impedance  $Z_0$ , as illustrated.



- (a) At  $t = 0$  the switch at  $z = D/2$  opens for  $D/10c$  seconds and then recloses. Sketch the voltage  $v(z)$  on the line at  $t = D/5c$ .
- (b) Will  $v_L(t)$  across the transistor load ever exceed its breakdown limit of  $7Z_0I_0$  volts? Briefly explain.

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.013 Electromagnetics and Applications  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.